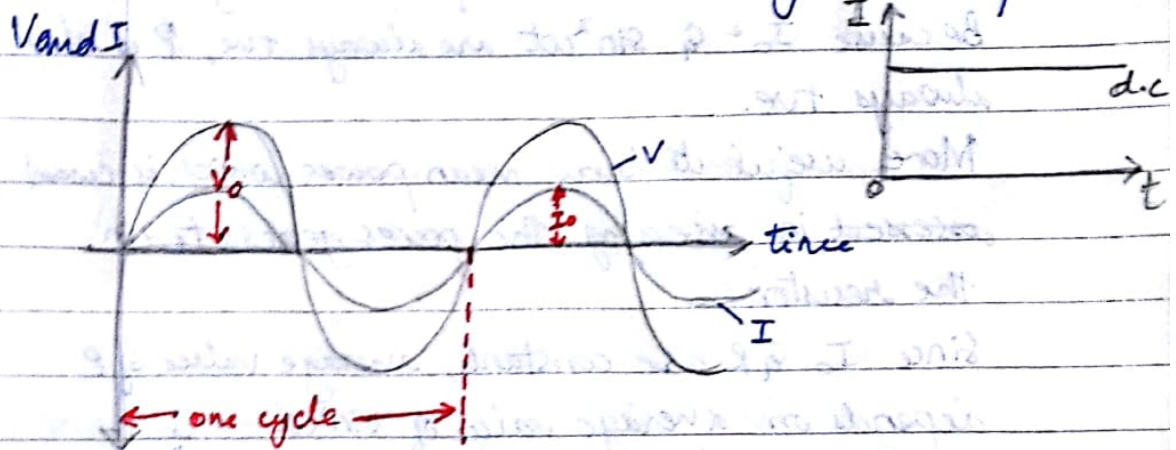


ALTERNATING CURRENTS

* Period: The time period T of an alternating p.d. or current is the time taken for one complete cycle.

* Frequency: The frequency f of an alternating p.d. or current is the number of cycles in one second.

* Peak values of voltage (V_0) and current (I_0) are their maximum values in a cycle i.e. amplitude.



Graph shows that:

- current & voltage varies cyclically
- i.e. half of the cycle, +ve & other half it is -ve.
- at any instant in time, I & V have a particular magnitude & direction given by the graph.
- V & I vary like a sine wave & \therefore described as sinusoidal.

• V & I are in phase.

• At time t ,

$$I = I_0 \sin \omega t$$

$$V = V_0 \sin \omega t$$

of the form $x = x_0 \sin \omega t$ for sinusoidal curve.

- * The peak value of the current or voltage is I_0 or V_0 , the amplitude of the oscillating current or voltage.
- * Peak-to-peak value is used, this means $2I_0$ or $2V_0$ or twice the amplitude.

* Power:

$$P = I^2 R \quad \text{but } I = I_0 \sin \omega t$$

$$\therefore P = I_0^2 R \sin^2 \omega t = \text{power @ any instant.}$$

Because I_0^2 & $\sin^2 \omega t$ are always +ve, P is also always +ve.

More useful to know mean power which is used assessed in assessing the power generated in the resistor.

Since I_0 & R are constants, average value of P depends on average value of $\sin^2 \omega t = \frac{1}{2}$

$$\therefore \langle P \rangle = \frac{1}{2} I_0^2 R = \frac{1}{2} V_0^2 R$$

This is half the maximum power.

Avg. value of square of current / p.d. ^{can} be used.

$$\langle I^2 \rangle = \frac{1}{2} I_0^2 \quad \text{and} \quad \langle V^2 \rangle = \frac{1}{2} V_0^2$$

* Root-mean-square (rms) values

→ aka effective value

→ equivalent to a steady direct current

→ d.c. of value $I =$ ac. of value I_{rms}

• The rms value of the current or voltage is that value of the direct current or voltage that would produce heat at the same rate in a resistor.

• The rms value of an ac is that steady current which delivers the same average power as the d.c. to a resistive load.

$$I_{rms} = \frac{I_0}{\sqrt{2}}$$

$$\text{rms value} = \frac{\text{peak value}}{\sqrt{2}}$$

$$V_{rms} = \frac{V_0}{\sqrt{2}}$$

$$* I_{rms} = \sqrt{\langle I^2 \rangle} = I_0 \sqrt{2} = 0.707 I_0$$

$$* V_{rms} = \sqrt{\langle V^2 \rangle} = V_0 \sqrt{2} = 0.707 V_0$$

$$V_{rms} = \langle V \rangle = \frac{V_0}{\sqrt{2}} \quad \langle I \rangle = \frac{I_0}{\sqrt{2}}$$


* Transformer

→ It is a pair of mutually inductive coils used to convey a.c. power from one coil to the other.

$$\rightarrow \frac{N_s}{N_p} = \frac{V_s}{V_p} = \frac{I_p}{I_s} \text{ for ideal transformer.}$$

$$P = V_p I_p = V_s I_s$$
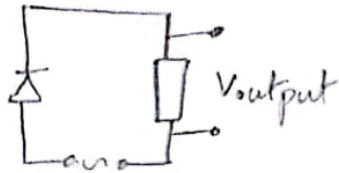
$$\therefore \frac{V_p}{V_s} = \frac{I_s}{I_p}$$




* Rectification is the process by which alternating current is converted to direct current.

→ Suppose a single diode is connected to an a.c. circuit → unidirectional flow of $I \Rightarrow$ output voltage across resistor will consist only of the +ve half cycles of the input voltage.

The diode has rejected the -ve part of the input, producing a unidirectional current that fluctuates considerably, rather than a d.c.

This is called half-wave rectification.

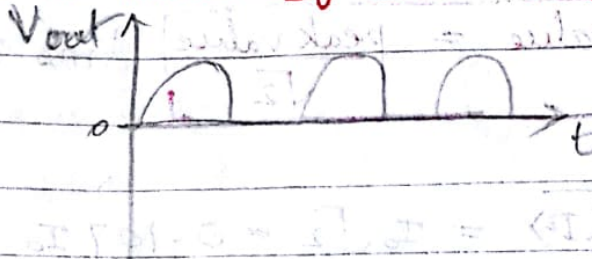

For one half of the time the voltage is zero & this means that the power available from a half-wave rectified supply is reduced.


→ To overcome this problem of reduced power, a bridge rectifier is used.

It is more satisfactory also to make use of the -ve half-cycles of the input & reverse their polarity. This process is called full-wave rectification.



can also use LEDs

The bridge-rectifier circuits:

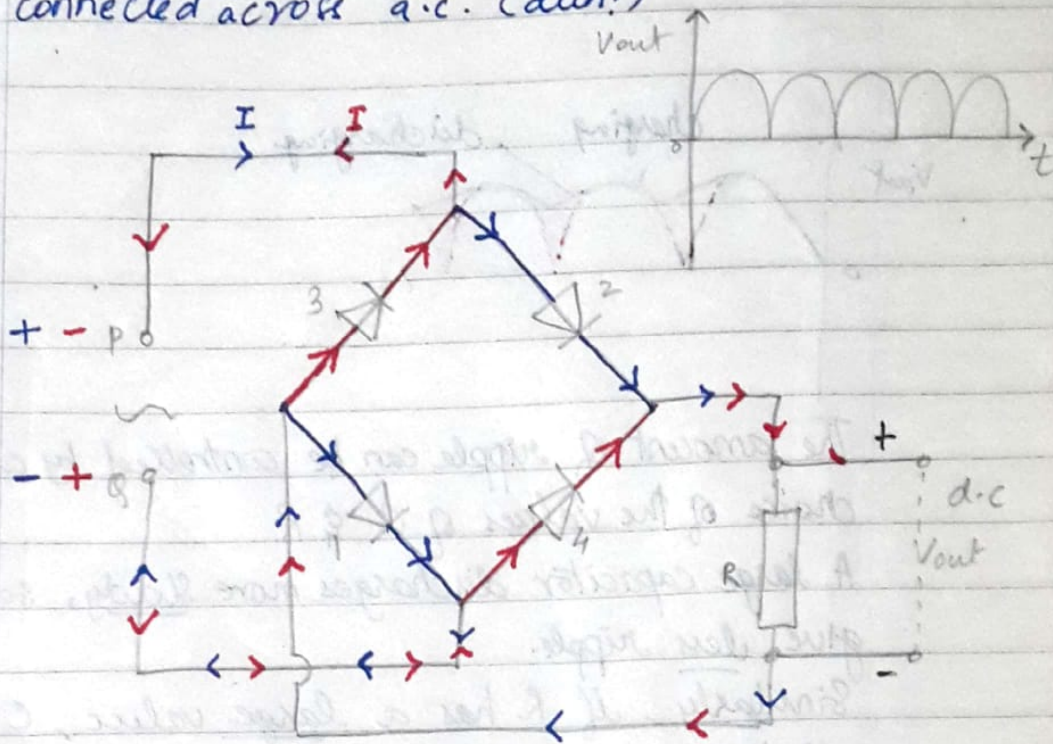- consists of 4 diodes
- arranged in a diamond pattern
- connected across a.c. (duh!)



- * Note that in both halves of the cycle, current flows the same way (downwards) through R , so the top end of R must be +ve.
- * The circuit has produced unidirectional current but the output is still not a good approximation to the steady d.c. required for most electronic equipment.
- * A capacitor is inserted across the output terminals of the bridge circuit. It charges up on the rising part of the half-cycle & then discharges as the V_{out} falls. The effect is to reduce the fluctuations in the unidirectional output. This process is called smoothing.

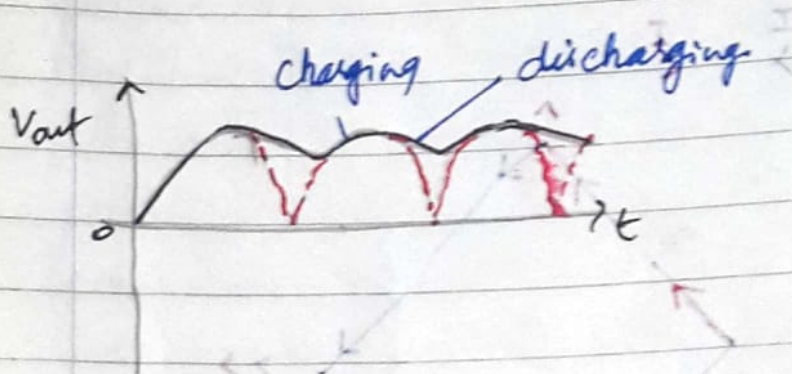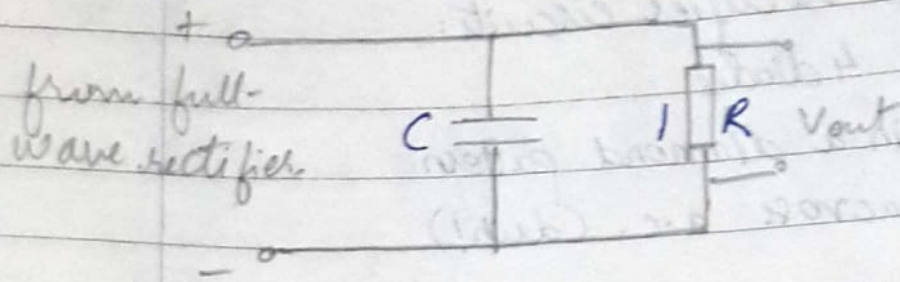

The amount of ripple can be controlled by careful choice of the values of C & R .

A large capacitor discharges more slowly, so will give less ripple.

Similarly, if R has a large value, C will discharge more slowly.

In practice, the greater the value of $R \times C$, the smoother the rectified a.c.

However, if R & C have large values, it will be difficult to change the value of the voltage quickly.