



CAPACITANCE

* Functions of capacitors in simple circuits:

- used to store electrical charge & energy
- used in computers: charged up in normal use & then gradually discharge if there is a power failure so that the comp. will operate long enough to save valuable data.
- also provides extra energy when needed such as using the flash in a camera - The capacitor connected to the bulb discharges rapidly to give a short but intense flash.
- a simple capacitor consists of 2 leads connected to 2 metal plates (where the charge is stored) with an air-gap between them which acts as an insulator. ⇒ "parallel-plate capacitor"
- the capacitance of an air-filled capacitor can be ↑ by putting an insulating material (mica/waxed paper) between the plates ⇒ "dielectric".
- in a type of capacitor called ~~etc~~ electrolytic capacitor, the dielectric is deposited by an electrochemical reaction.
- These capacitors must be connected with the correct polarity for their plates or they will be damaged.
- Capacitor:  Electrolytic capacitor: 

* The capacitance of a capacitor is the charge stored per unit of potential difference across it.

$$\text{Capacitance (C)} = \frac{\text{Charge (Q)}}{\text{p.d. (V)}}$$

* Capacitance is the ratio of charge to potential for a conductor.

* Unit: Farad (F) = one coulomb per volt. ($F = CV^{-1}$)

* Energy stored in a capacitor:

→ When charging, work is done by the battery to ~~move~~^{move} charge on to the capacitor.

→ Energy is transferred from the power supply & stored as Electrical P.E. in the capacitor.

→ $Q \propto V$ & $\therefore Q = CV$ where C is the constant of proportionality

→ W (work done) (and E_p) = QV

$\therefore \Delta E_p = V_0 \Delta q = \text{area under } V\text{-Charge graph.}$

* The energy transferred from the battery when a capacitor is charged is given by the area under the graph line when charge (x-axis) is plotted against potential difference (y-axis).

* Because the graph is a straight line through the origin,
 $E_p = \frac{1}{2} QV$

$$E_p = \frac{1}{2} QV = \frac{1}{2} CV^2 = \frac{Q^2}{2C}$$

* Factors affecting capacitance

1. Dielectric material
2. Area of plates (A)
3. Dis Separation of plates (d)

$$\rightarrow C \propto \frac{A}{d}$$

→ For a capacitor with air or a vacuum between the plates, the constant of proportionality is the permittivity of free space.

$$\therefore C = \frac{\epsilon_0 A}{d}$$

* Since the use of a dielectric \uparrow the capacitance, we introduce a quantity called the "relative permittivity" ϵ_r of a dielectric.

"The relative permittivity is defined as the capacitance of a parallel-plate capacitor with the dielectric between the plates divided by the capacitance of the same capacitor with a vacuum between the plates." $= \frac{C_{di}}{C_{va}} = \epsilon_r$

$$\therefore C = \frac{\epsilon_0 \epsilon_r A}{d}$$

* Capacitors in series & parallel.

Parallel: (like resistors opposite):


$$C_{total} = C_1 + C_2 + C_3 \dots$$

→ The combined capacitance is the sum of their individual capacitances.

→ This is because, when 2 capacitors are connected in parallel together, they are equivalent to a single capacitor with larger plates. ↑ size of plates → ↑ area for charge build-up → ↑ capacitance.

→ The total charge Q stored by 2 capacitors connected in parallel & charged to a potential difference V is given by:

$$Q = C_{\text{total}} \times V$$

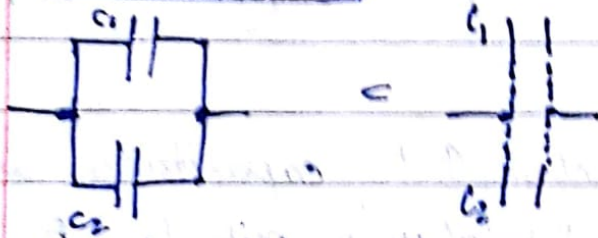

→ Derivation

• Since in parallel, V is the same:

$$Q_1 = C_1 V \quad \& \quad Q_2 = C_2 V$$

• Total charge stored = sum of these.

$$Q = Q_1 + Q_2 = C_1 V + C_2 V \quad \rightarrow \text{conservation of charge!}$$

• Since V is a common factor

$$Q = (C_1 + C_2) V$$

• Comparing this with $Q = C_{\text{total}} V$ gives the required

$$C_{\text{total}} = C_1 + C_2$$

OR $Q = CV = (C_1 + C_2) V$

$$\frac{CV}{V} = C_1 + C_2 \quad \therefore \boxed{C = C_1 + C_2}$$

SERIES

→ Combined capacitance = $\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} \dots$

→ $V = \frac{Q}{C}$ & in series $V = \underline{V_1 + V_2}$ addition of pds.

$\therefore \frac{Q}{C} = \frac{Q}{C_1} + \frac{Q}{C_2}$ ⊕ where each capacitor has charge Q as current is same in series.

Derivation

$\frac{Q}{C} = Q \left(\frac{1}{C_1} + \frac{1}{C_2} \right)$

Also: conservation of charge in series.

$\frac{Q}{C} \times \frac{1}{Q} = \frac{1}{C_1} + \frac{1}{C_2} \quad \therefore \frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2}$

- The reciprocal of the combined capacitance equals the sum of the reciprocals of the individual capacitances in series.
- For 2 identical capacitors in series, the combined capacitance is equal to half of the value of each one.
- For capacitors in series, the combined capacitance is ALWAYS LESS than the value of the SMALLEST individual capacitance.

* Capacitance of isolated bodies:

→ A conducting sphere of radius 'r' insulated from its surroundings & carrying a charge 'Q' will have a potential at its surface of 'V' where

$$V = \frac{1}{4\pi\epsilon_0} \frac{Q}{r}$$

$$V = \frac{kQ}{r}$$

$$F = \frac{kQ_1 Q_2}{r^2}$$

$$F = \frac{qV}{r} = F = \frac{QV}{r} = \frac{kQ_1 Q_2}{r^2}$$

$$V = \frac{kQ_1 Q_2 r}{Q_1 r^2}$$

$$\therefore V = \frac{kQ}{r}$$

Since $C = \frac{Q}{V}$, it follows that the capacitance of a sphere is

$$C = 4\pi\epsilon_0 r \quad \text{because} \quad C = \frac{Q}{V} = \frac{Q \times r}{\frac{kQ}{r}} = \frac{r}{\frac{1}{4\pi\epsilon_0}}$$

$$= \frac{r \times 4\pi\epsilon_0 r}{r}$$

$$\therefore \boxed{C = 4\pi\epsilon_0 r}$$